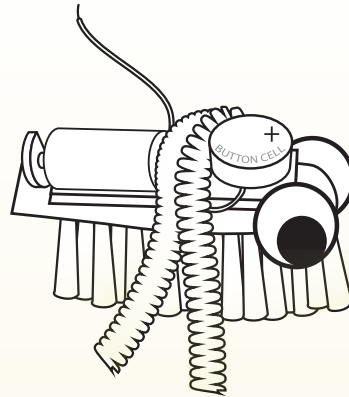


Name _____

Class/Date _____

Draw a Circuit

Student Worksheet



Directions: Draw a circuit and label the following parts:

- Motor
- Battery
- Switch
- Positive
- Negative